
 


 
Approach: I first gave input to rom then the output from rom gets stored in a register in one half cycle then in next cycle , rom receives the input as previous input +1.




After travelling in forward direction, once we get 255, the number in adder is changed from 1 to 2 and we traverse in backward direction in list.



 The data and address is stored in registers.



 After storing in the register, Comparator is used to determine the minimum address and corresponding to that data , address is also given as output. If data is same, minimum address is given as output.



Components	Quantity		
ROM	1	75	
74179	7	14	
74161	1	2	
7474	10	10	
Comparator	4	8	
clock	2	80	
Logic Gates(2 i/p)			
subadder	18		
selector1	16		
selector2	16		
And8_4	1		
not	4		
MIN	47		
Selectline	35		
	118	11.8	
Logic Gates(3 i/p)			
MIN	5		
AND8	3		
	8	1.6	
COST		202.4	